


# Ladder Logic Fundamentals

Industrial Control Systems  
Fall 2006

# Purpose of Industrial Controls

- In general, the purpose of an industrial control system is to control a process or mechanical system
- Examples include:
  - Beer brewing, camshaft machining, press loading, automobile body welding, tube cutting, foam curing, water pump assembly, automobile painting, truck frame coating, etc.


# Components of Control

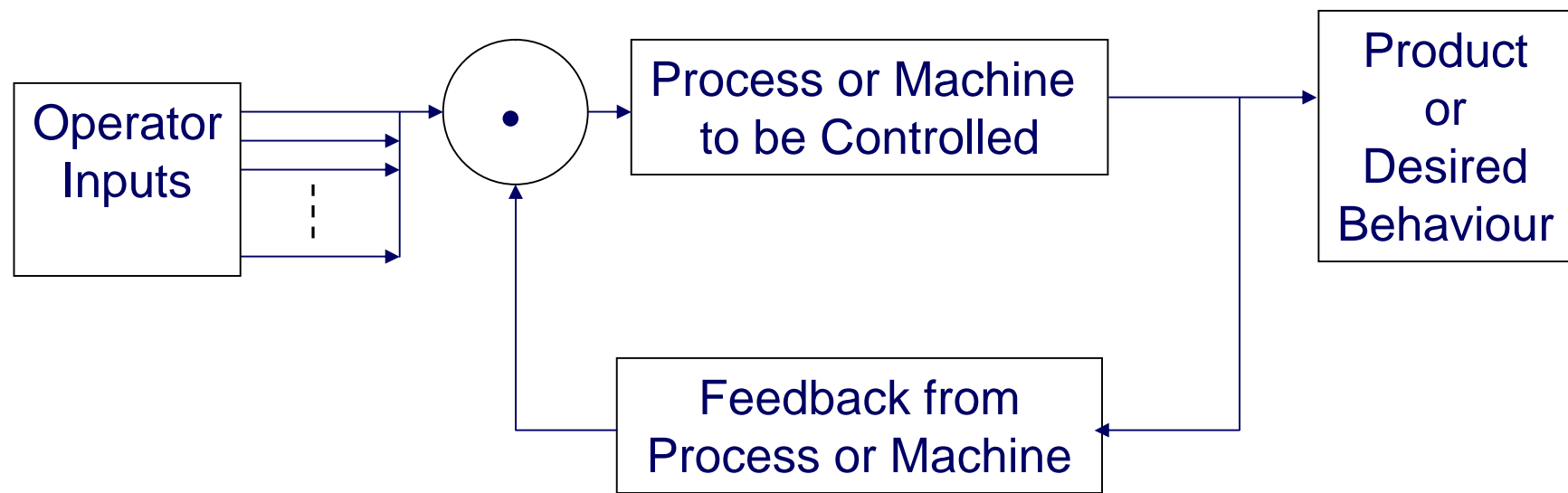

# History

- Before the use of computers, industrial control systems were implemented as mechanical, pneumatic/hydraulic or electric circuits
- Hardwired switches and electromechanical relays implemented the desired control logic
- Today, relay panels are still used in applications with low complexity.
- More often, I/O devices interface with a PLC that implements the desired logic.

# Relay Panel

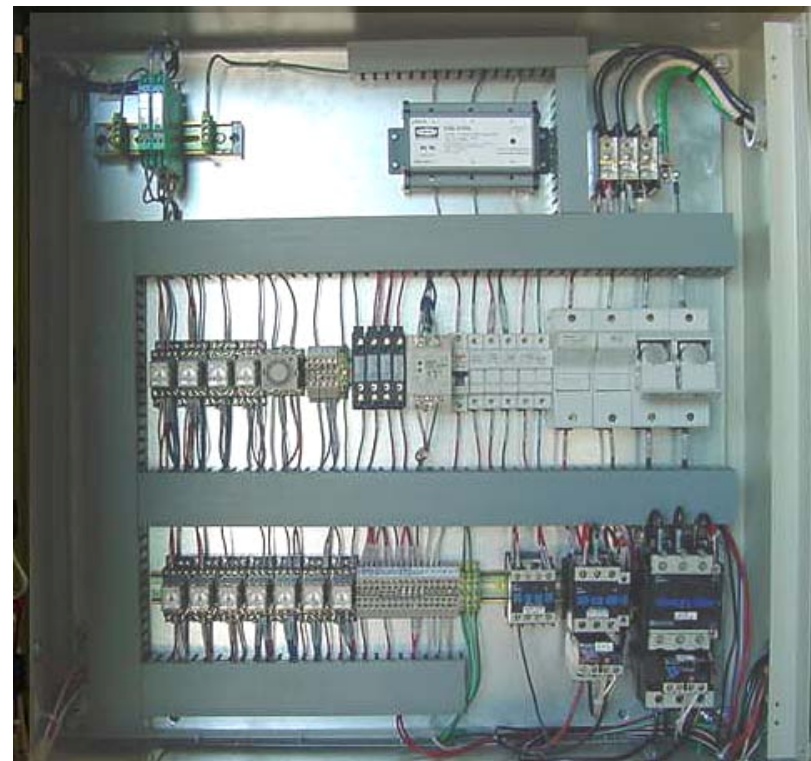


<http://www.maple-leaf.ca/indrelaybasedcontrol.html>

# Control Supply Transformers


- Unlike high voltage (i.e. 240 VAC, 480 VAC, 575 VAC) output devices such as motors, the control systems are powered by lower voltage levels.
- Depending on the application, the control voltage can be 24 VDC or 120 VAC.
- The control logic supply is usually derived from the higher line voltages using a transformer.

# Control Supply Transformers

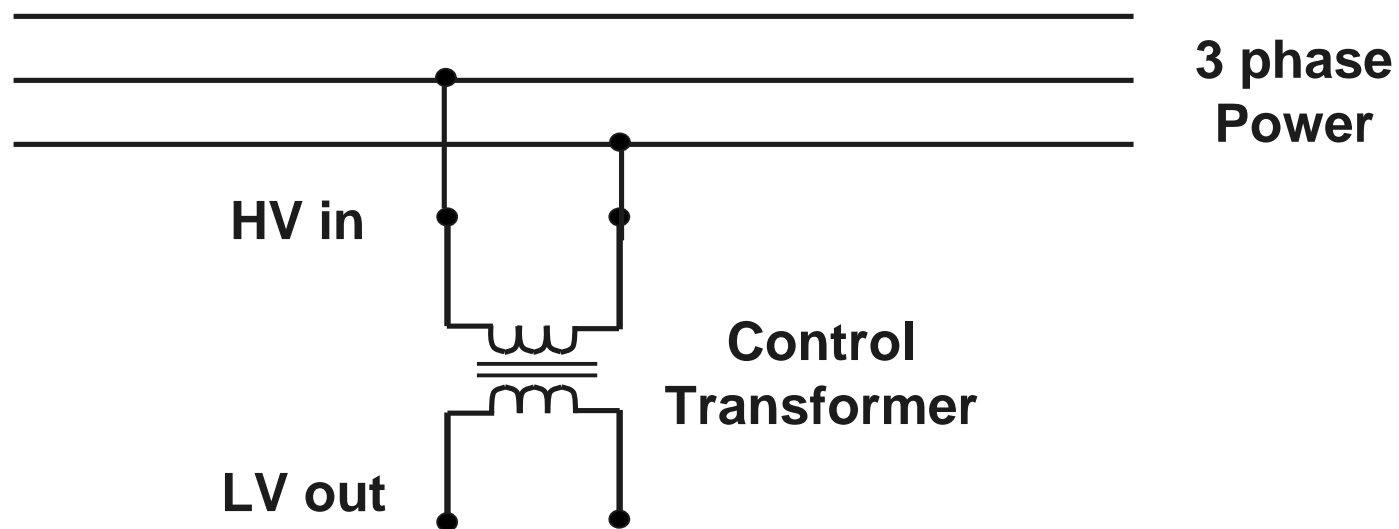
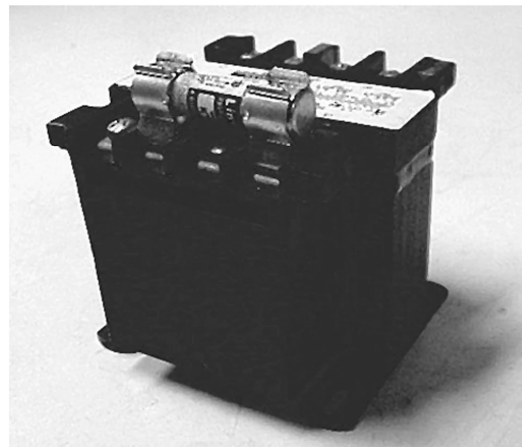
# Fuses

- Control circuits are always fuse protected
- This will prevent damage to the control transformer in the event of a short circuit






# Fuses


- Fuses should be immune to current transients (slow blow)
- Must be rated at a current that is less than or equal to the rated secondary current of the control transformer
- The fusing of control circuits can be complex. There are many different fuse types with trip characteristics available.


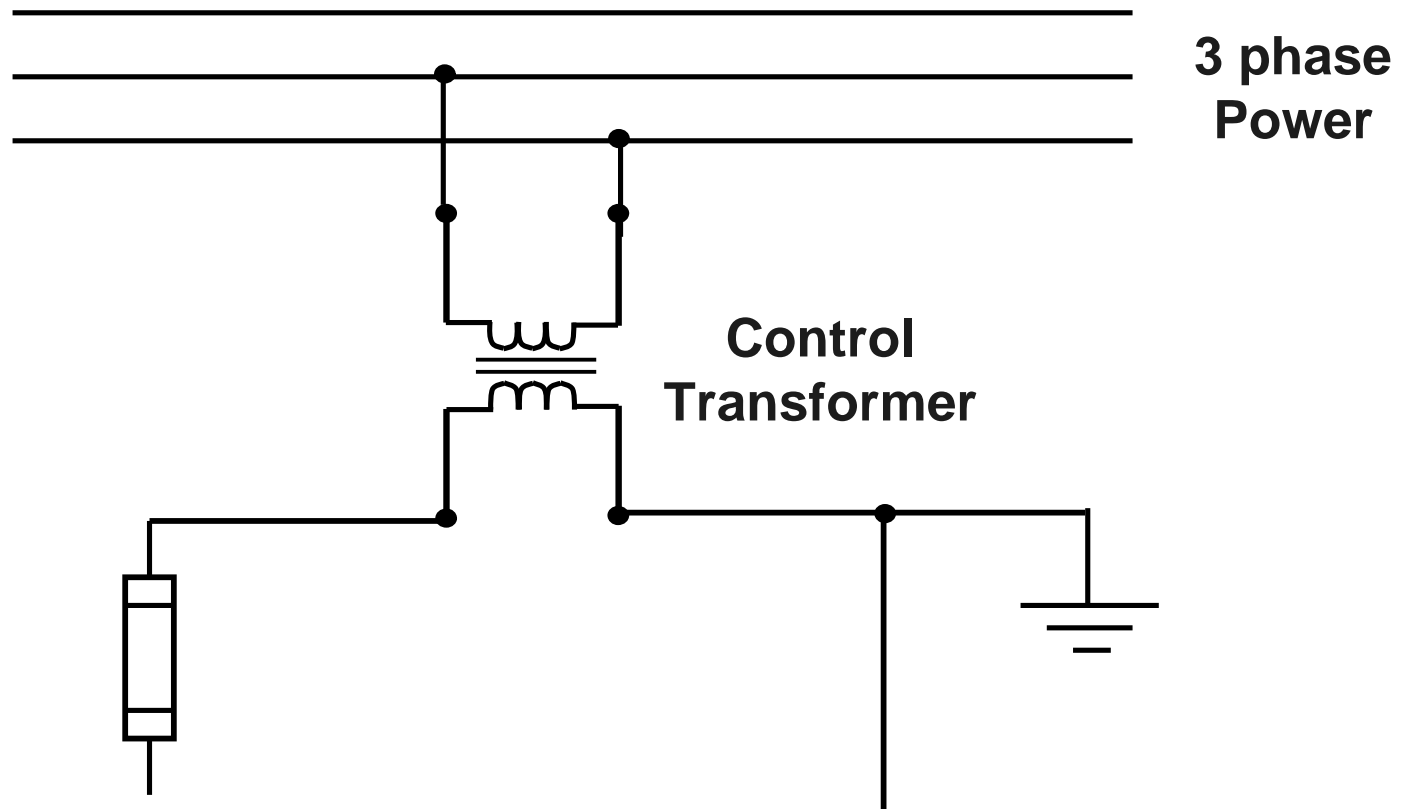
# Typical Diagram of Control Circuit Power




# Ladder Logic

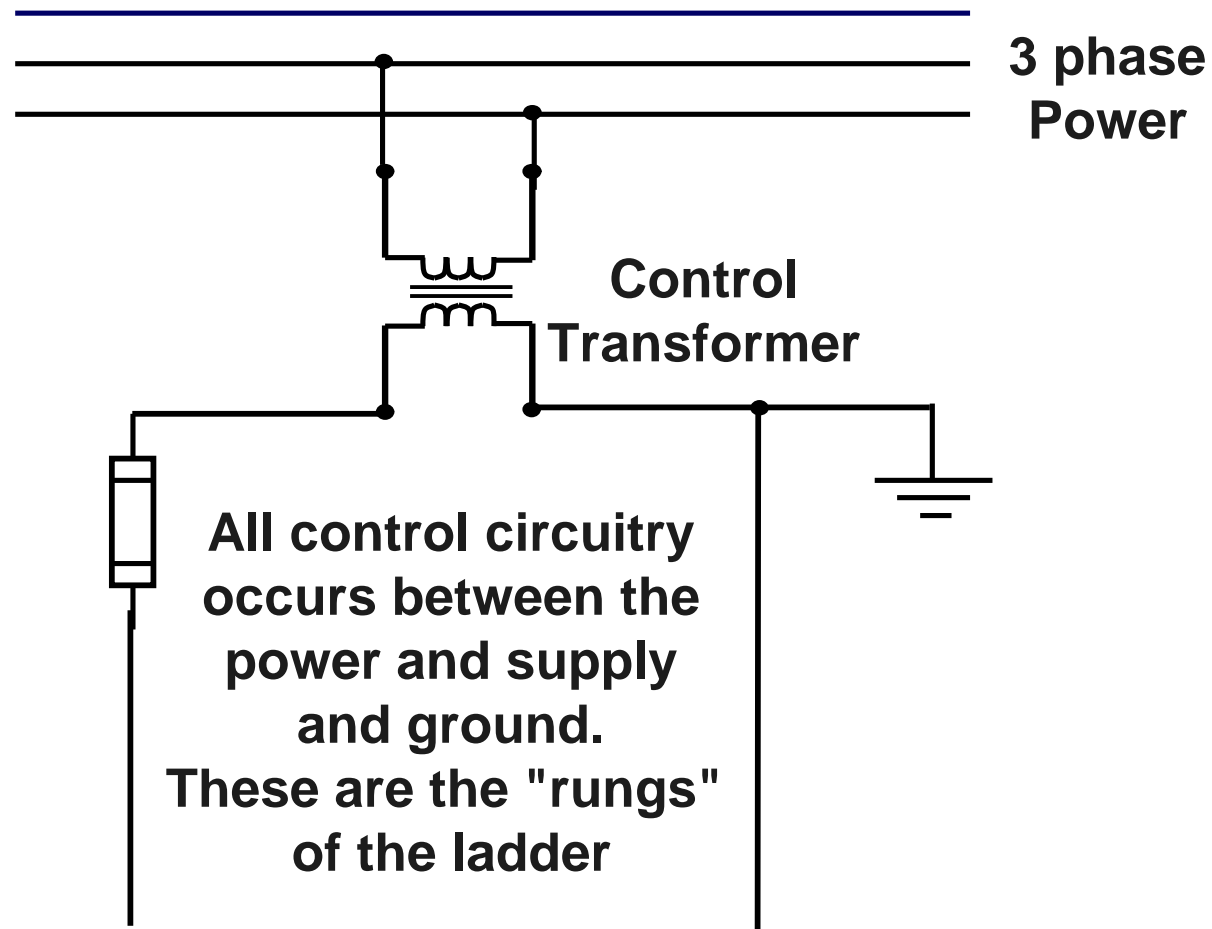

# Boolean (combinational) Logic and Relay Logic

- Switches and relays in a machine perform some type of control operation “logical function” such as AND, OR, NOT as found in digital circuits
- Coils, N/O and N/C contacts can be wired to perform logical functions
- No storage of previous states


# Ladder Logic - AND Function

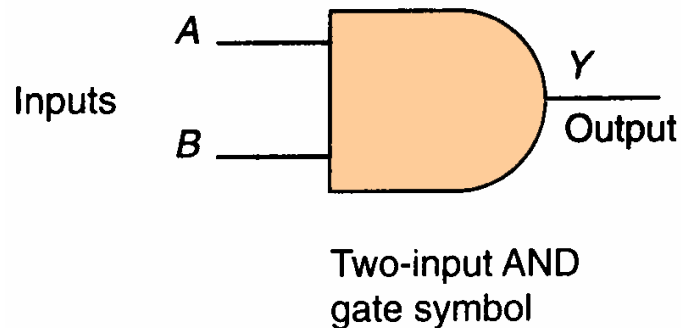

Inputs		Output
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

- Binary 1 represents the presence of a signal or the occurrence of some event, while binary 0 represents the absence of the signal or nonoccurrence of the event.
- For example, the closing of a switch would represent a logic 1, while an open switch represents a logic 0.


# Ladder Logic – AND Function

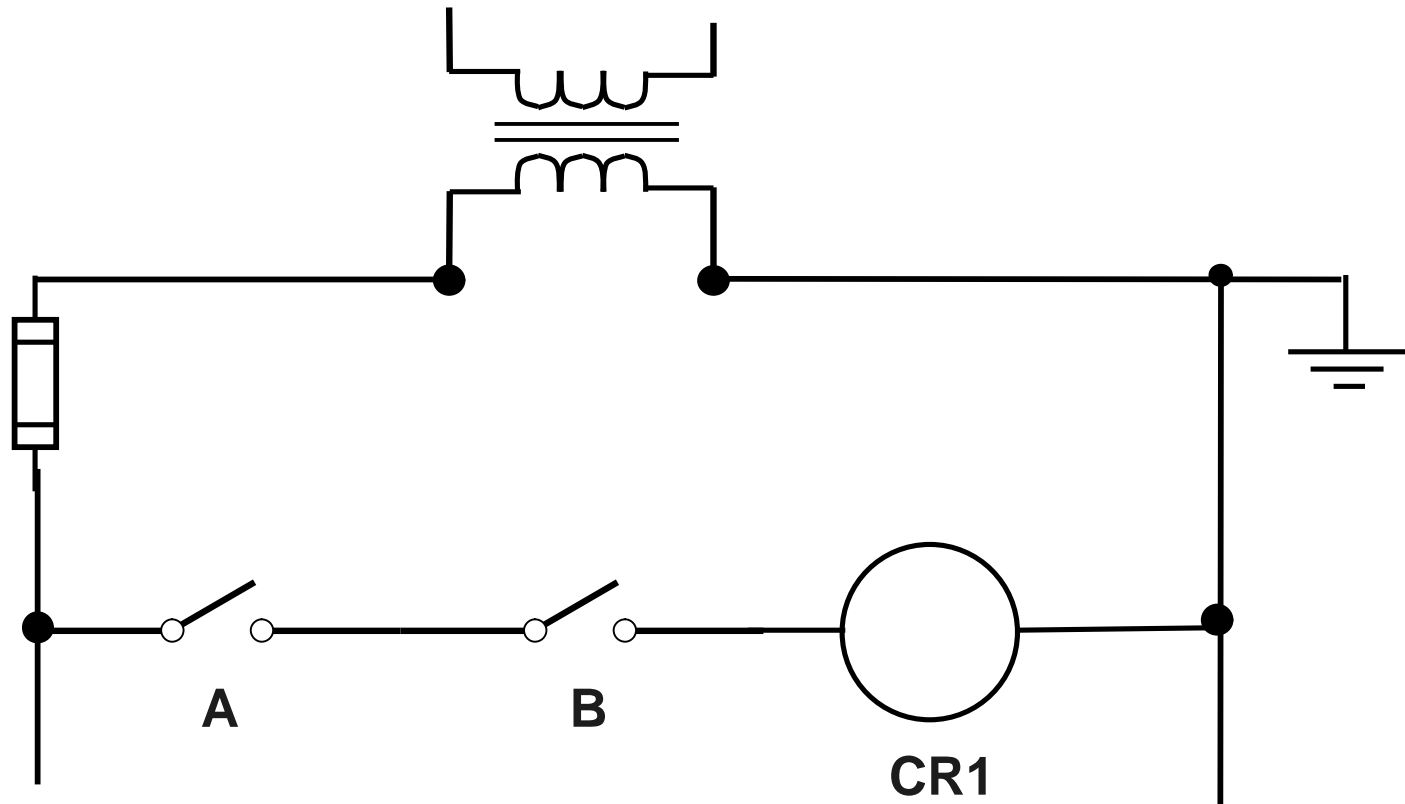


**Both A AND B must be closed to energize CR1**
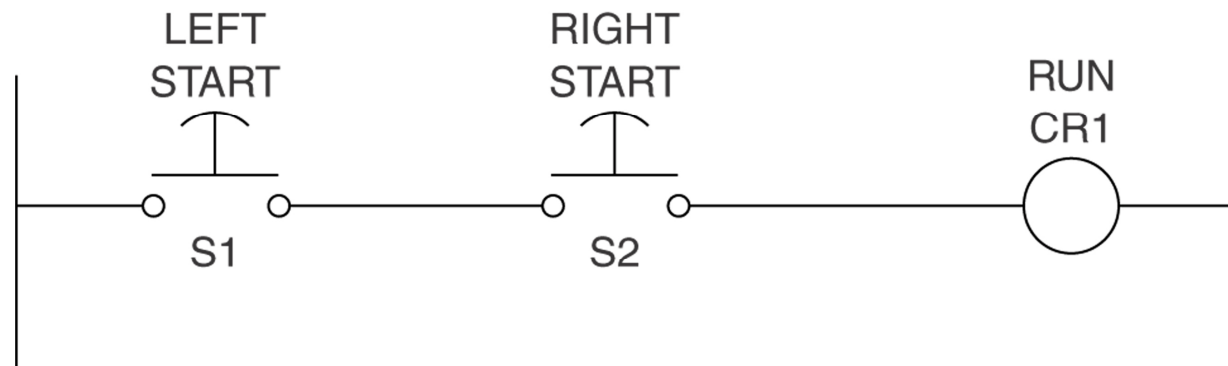
# Application of AND Logic

- Press operation
- The machine can be only cycled by pressing two switches simultaneously using two hands



# Ladder Logic - OR Function

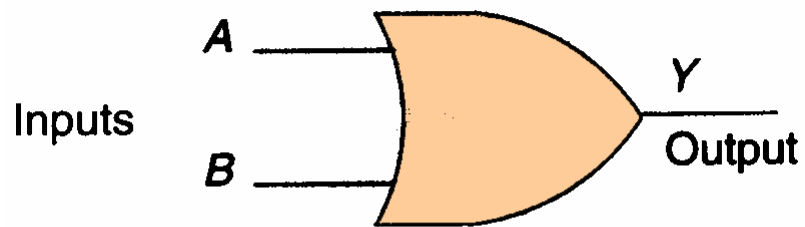


Two-input OR  
gate symbol

OR truth table

Inputs		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1




# Ladder Logic – OR Function

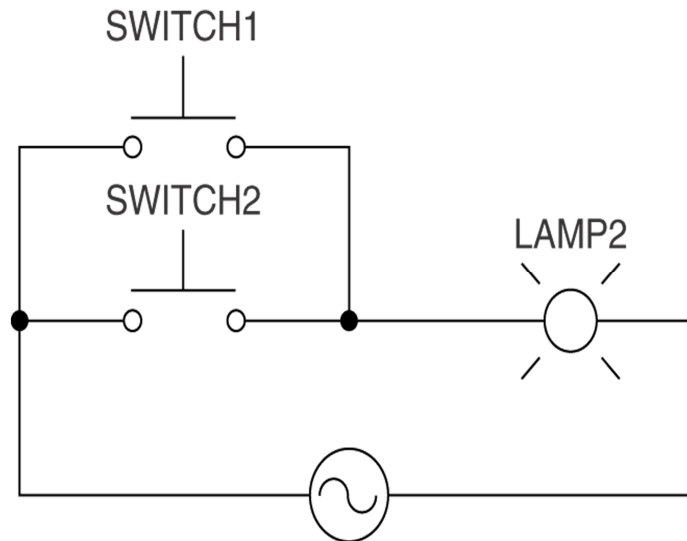

- The lamp is on if SWITCH1 OR SWITCH 2 is closed.


# Ladder Logic – NOT Function

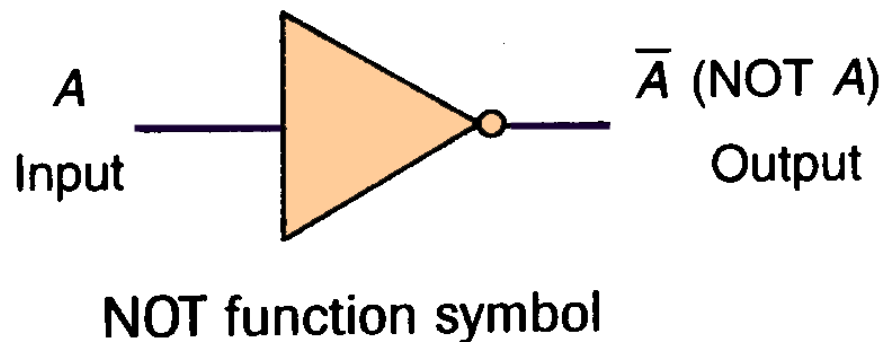

A	NOT A
0	1
1	0


- The output is the inverse of the input

# Ladder Logic – NOT Function

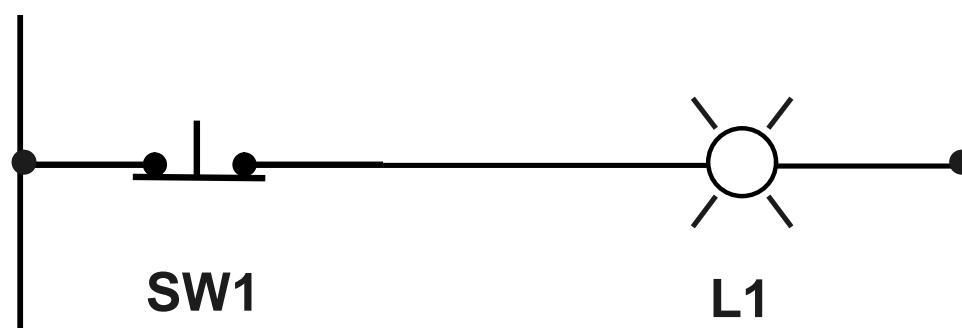


- The light is on when the switch is open

# Ladder Logic – XOR Function

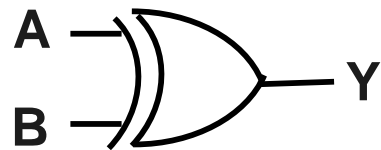

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

# Ladder Logic – XOR Function

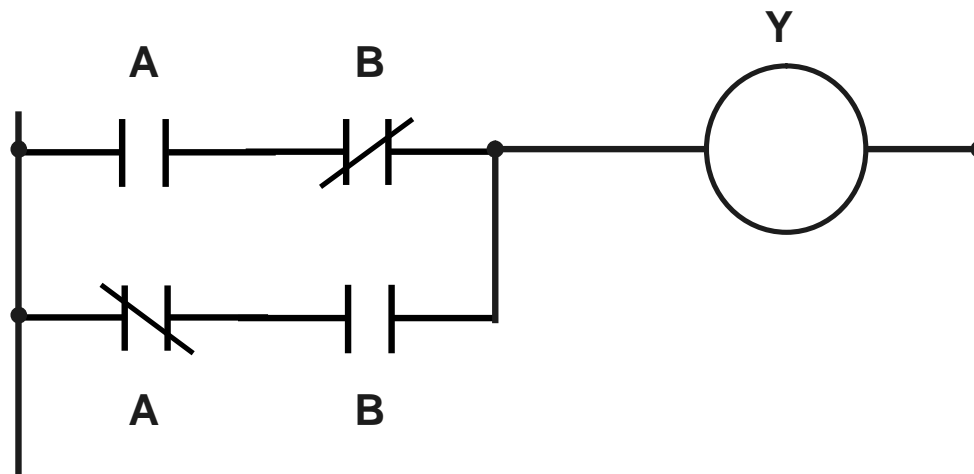


# Sequential Logic

- Previous state used along with state present inputs to determine output.  
present state
- SR, D, and T flip flops
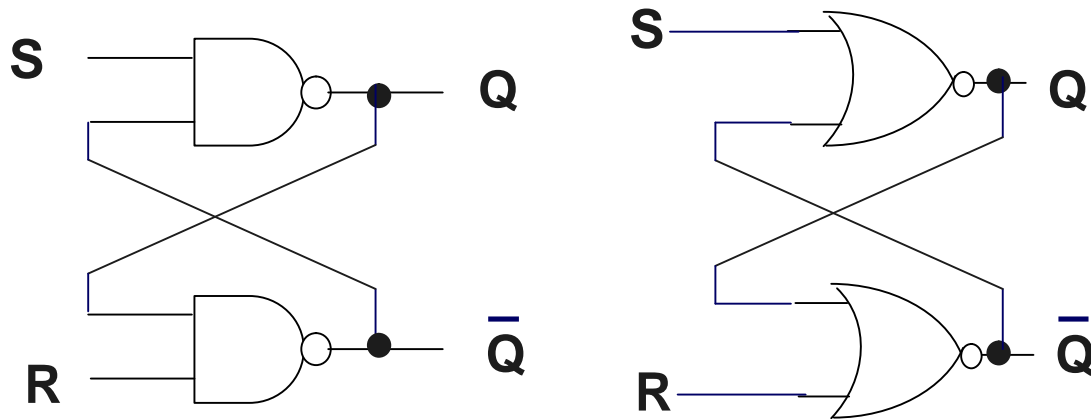
# The SR Latch


- The SR latch has 2 stable states, on and off
- The S, or set input is used to turn on the output. The R, or reset input is used to turn off the output.



S	R	Q
0	0	$Q_{(t-1)}$
0	1	0
1	0	1
1	1	Race
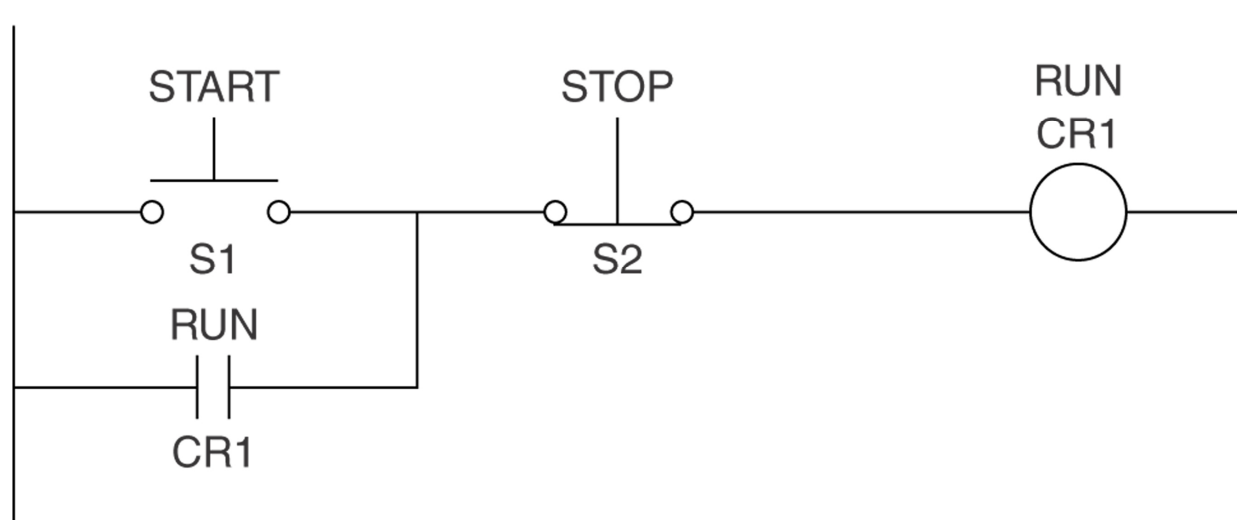
# The SR Latch

- Occasionally, it is necessary to latch a relay ON when the activating device goes OFF.
- An SR latch may be formed by a NO and NC switch.
- The start button is the set input, while the stop button is the reset input.
- The physical act of pushing the start or stop button is analogous to applying a logic 1 to the S, or R inputs respectively.






# The T Flip Flop

- Sometimes it is useful to have a momentary contact switch the output on during the first switch contact, and switch the output off during the second switch contact.

# T Flip-Flop Proposed Circuit

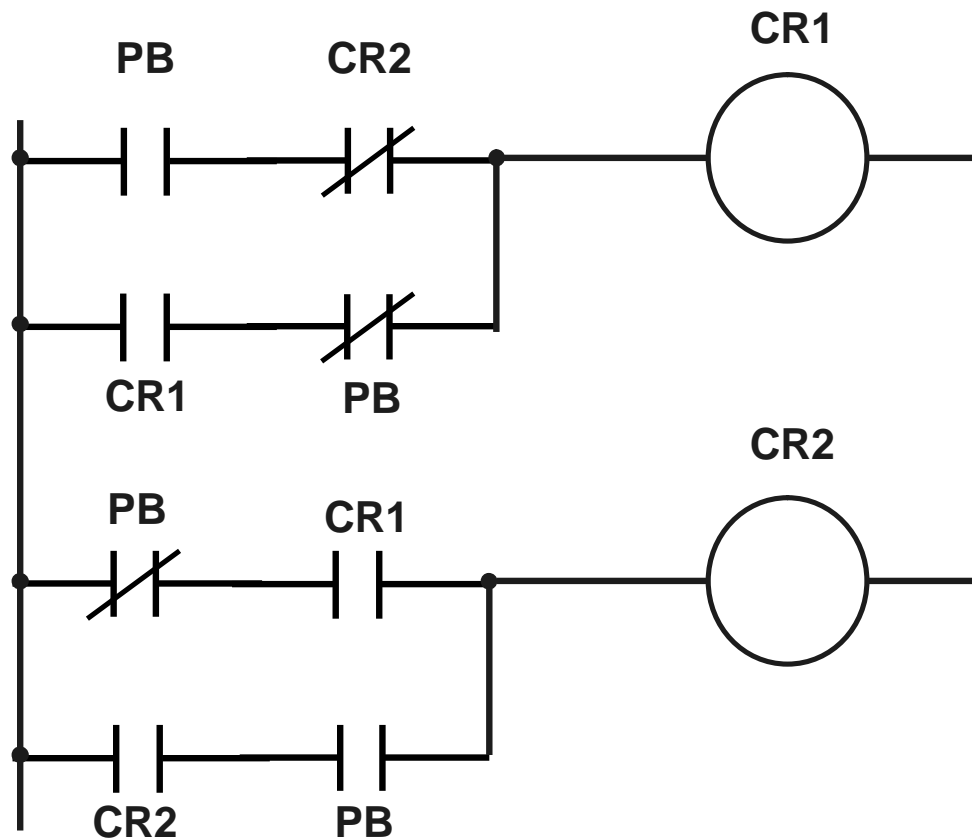

Output appears on CR2

# T Flip-Flop

- Homework – Verify that the circuit on the previous page works through an analysis of the circuit states.
- Explain the operation of the circuit.


# Anti-Tie Down and Anti-Repeat

- The machine must not have the capability to be cycled by tying down one of the two RUN switches and using the second to operate the machine
- In most cases this is an extremely hazardous practice
- Anti-tie down and anti-repeat solve this problem

# Anti-Tie Down and Anti-Repeat


- Both switches must be pressed at the same time within small time window
- If one switch is pressed then the other is pressed after the time is expired, the machine will not cycle
- We need:
  - Two switches
  - TON relay

# Anti-Tie Down and Anti-Repeat

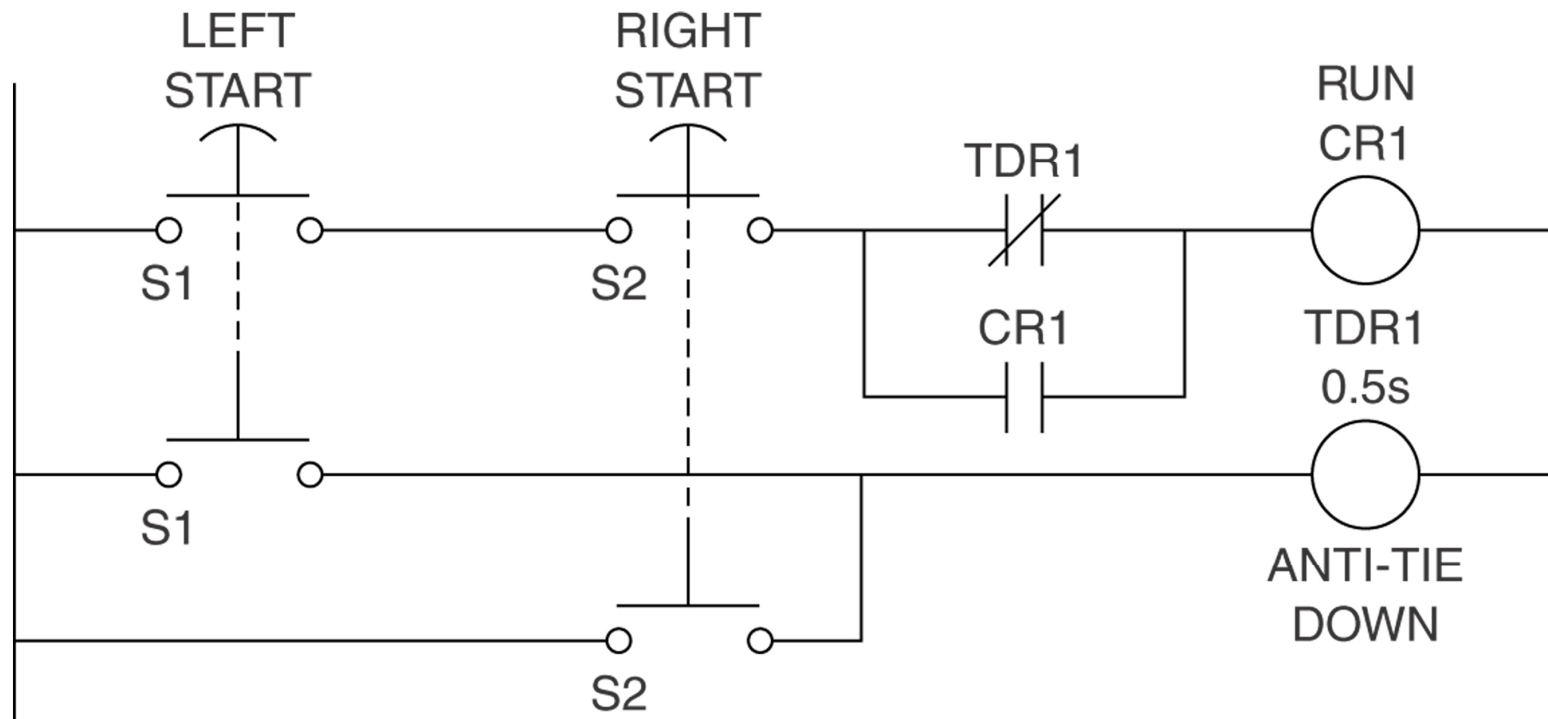

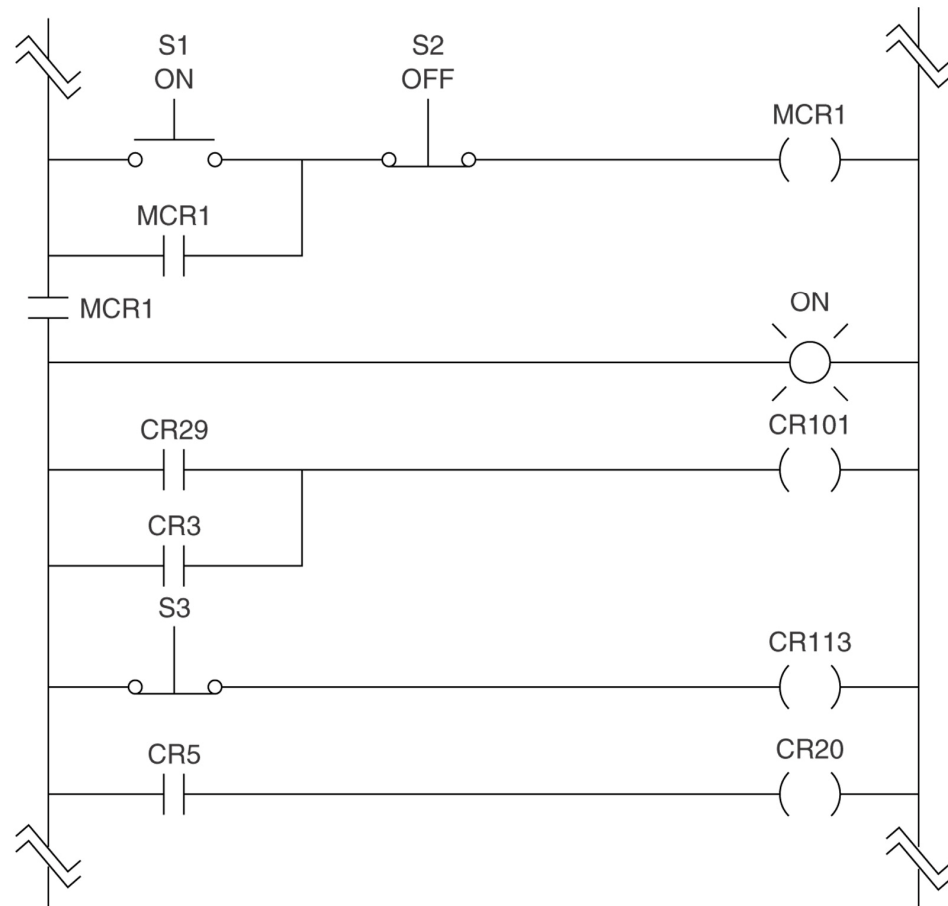
# Master Control Relays (MCRs)

- Used to enable or disable entire sections of control circuit (rungs)


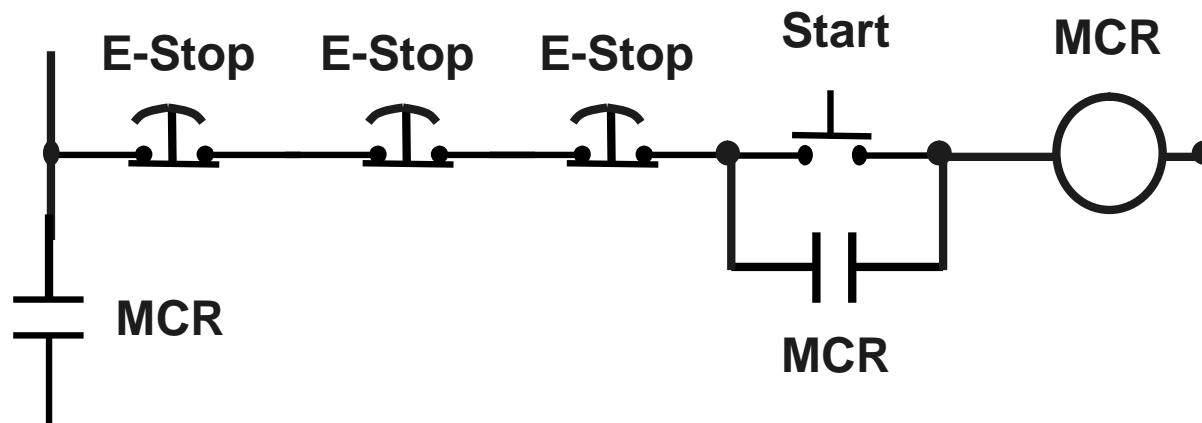
# MCR's – Emergency Stops


- Typically, MCR's are used in Emergency Stop (E-Stop) circuits to disable power to a circuit or machine in the event of a fault, or an operator initiated stop.






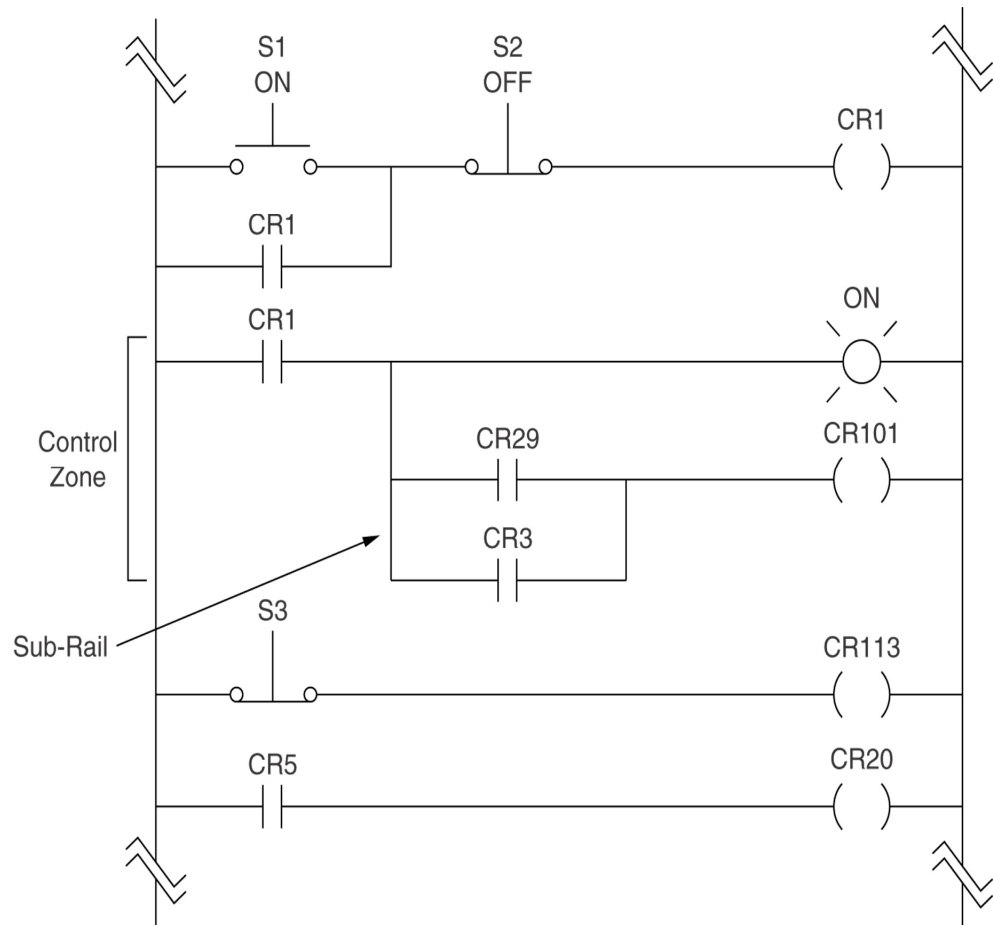
# Control Zones

- Used to apply control to specific sections of the control circuitry


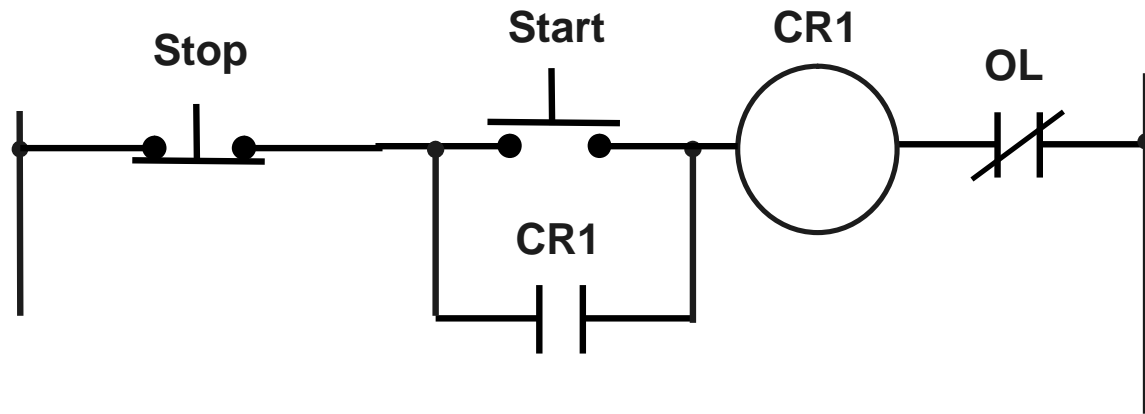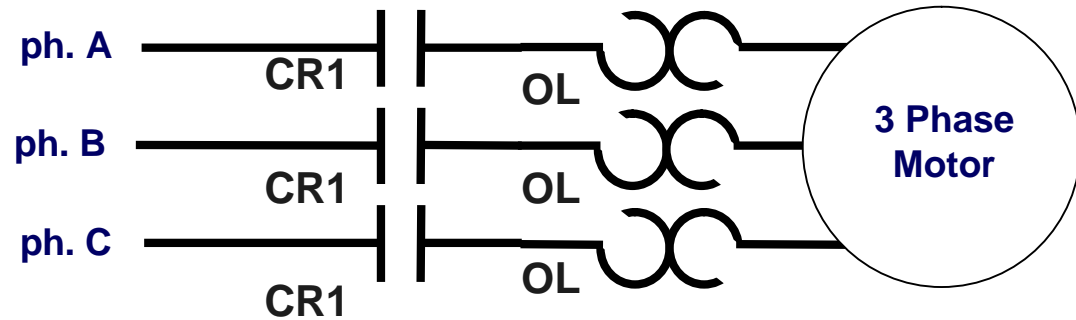
# Motor Starter Wiring

- A 3 phase motor can be started in the following manner:



## Motor Starter Wiring – Single Phase Motors

- Homework: Investigate how a three phase motor starter can be used to control a single phase motor.